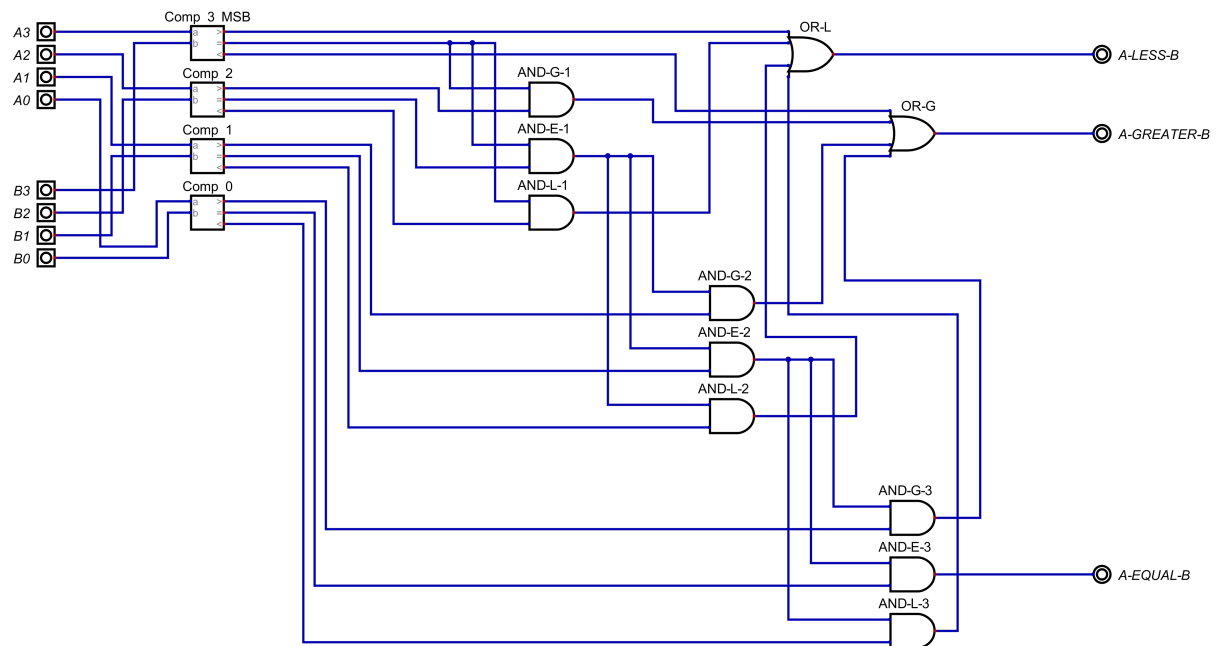


PRE-LAB #3 Report

Berna Yıldiran 26431

Circuit Design

As the initial step of this lab project, the “4-Bit Signed Comparator Circuit” is designed using Digital software. The circuit design can be seen in Figure 1.



Circuit Flow

Step 1: MSBs (A3 and B3) of the input A and B is compared using 1-bit comparator (Comp 3 MSB).

- If $A_3 > B_3$, the output will be sent to OR-L GATE before the A-LESS-B output. (w1)
- If $A_3 = B_3$, the output will be sent to AND-G-1, AND-E-1, AND-L-1 GATES, in order to add the result of $A_2 - B_2$ comparison to the circuit to decide the final output. (w2)
- If $A_3 < B_3$, the output will be sent to OR-G GATE before the A-GREATER-B output. (w3)
- NOTE: Since A and B are signed integers, and 1 represent negative numbers and 0 represent positive numbers, while $A(1) > B(0)$ the wire connects to the OR-L GATE before the A-LESS-B output. In the same way, when $A(0) < B(1)$ the wire connects to the OR-G GATE before the A-GREATER-B output.

Step 2: When MSBs of A and B are equal, the circuit compares A2 and B2 bits of the inputs using 1-bit comparator (Comp 2).

- If $A_2 > B_2$, the output will be sent to AND-G-1 GATE together with w_2 and the result of this operation will be connected to the OR-G GATE before the A-GREATER-B output. (w_4)
- If $A_2 = B_2$, the output will be sent to AND-E-1 GATE together with w_2 and the result of this operation will be sent to AND-G-2, AND-E-2, AND-L-2 GATES, in order to add the result of $A_1 - B_1$ comparison to the circuit to decide the final output. (w_5)
- If $A_2 < B_2$, the output will be sent to AND-L-1 GATE together with w_2 and the result of this operation will be connected to the OR-L GATE before the A-LESS-B output. (w_6)

Step 3: If first two bits of A and B are equal, the circuit compares A_1 and B_1 bits of the inputs using 1-bit comparator (Comp 1).

- If $A_1 > B_1$, the output will be sent to AND-G-2 GATE together with w_6 and the result of this operation will be connected to the OR-G GATE before the A-GREATER-B output. (w_7)
- If $A_1 = B_1$, the output will be sent to AND-E-2 GATE together with w_6 and the result of this operation will be sent to AND-G-3, AND-E-3, AND-L-3 GATES in order to add the result of $A_0 - B_0$ comparison to the circuit to decide the final output. (w_8)
- If $A_1 < B_1$, the output will be sent to AND-L-2 GATE together with w_6 and the result of this operation will be connected to the OR-L GATE before the A-LESS-B output. (w_9)

Step 4: If first three bits of A and B are equal, the circuit compares A_0 and B_0 bits of the inputs using 1-bit comparator (Comp 0).

- If $A_0 > B_0$, the output will be sent to AND-G-3 GATE together with w_8 and the result of this operation will be connected to the OR-G GATE before the A-GREATER-B output. (w_{10})
- If $A_0 = B_0$, the output will be sent to AND-E-3 GATE together with w_8 and the result of this operation will sent to output A-EQUAL-B. (w_{11})
- If $A_0 < B_0$, the output will be sent to AND-L-3 GATE together with w_8 and the result of this operation will be connected to the OR-L GATE before the A-LESS-B output. (w_{12})

Step 5: Depending on the input wires of OR-G and OR-L GATES, the output of the circuit based on the input A and B will be determined.

- Based on the values of w_1, w_6, w_9, w_{12} , which are the inputs of the OR-L GATE, if any of the inputs are 1, the circuit will output the result of A - B comparison as A-LESS-B.
- Based on the values of w_3, w_4, w_7, w_{10} , which are the inputs of the OR-G GATE, if any of the inputs are 1, the circuit will output the result of A - B comparison as A-GREATER-B.

Verilog: Design Sources

The source code of the above circuit is written in Verilog as the following:

```

`timescale 1ns / 1ps
module CompUnsigned #(
    parameter Bits = 1
)
(
    input [(Bits -1):0] a,
    input [(Bits -1):0] b,
    output \> ,
    output \= ,
    output \<
);
    assign \> = a > b;
    assign \= = a == b;
    assign \< = a < b;
endmodule

module Comparator_Signed_4Bit(
    input A3,
    input A2,
    input A1,
    input A0,
    input B3,
    input B2,
    input B1,
    input B0,
    output A_GREATER_B,
    output A_LESS_B,
    output A_EQUAL_B
);

    wire s0;
    wire s1;
    wire s2;
    wire s3;
    wire s4;
    wire s5;
    wire s6;
    wire s7;
    wire s8;
    wire s9;
    wire s10;
    wire s11;
    wire s12;
    wire s13;

    // -----
    // Comp 3 MSB
    CompUnsigned #(
        .Bits(1)
    )
    CompUnsigned_i0 (
        .a( A3 ),
        .b( B3 ),
        .\> ( s0 ),
        .\= ( s1 ),
        .\< ( s2 )
    );

    // -----
    // Comp 2
    CompUnsigned #(
        .Bits(1)
    )
    CompUnsigned_i1 (
        .a( A2 ),
        .b( B2 ),
        .\> ( s3 ),

```

```

        .\= ( s4 ),
        .\< ( s5 )
    );

    // -----
    // Comp 1
    CompUnsigned #(
        .Bits(1)
    )
    CompUnsigned_i2 (
        .a( A1 ),
        .b( B1 ),
        .\> ( s6 ),
        .\= ( s7 ),
        .\< ( s8 )
    );

    // -----
    // Comp 0
    CompUnsigned #(
        .Bits(1)
    )
    CompUnsigned_i3 (
        .a( A0 ),
        .b( B0 ),
        .\> ( s9 ),
        .\= ( s10 ),
        .\< ( s11 )
    );

    // -----
    // OUTPUTS
    assign s12 = (s1 & s4);
    assign s13 = (s12 & s7);
    assign A_EQUAL_B = (s13 & s10);
    assign A_LESS_B = (s0 | (s1 & s5) | (s12 & s8) | (s13 & s11));
    assign A_GREATER_B = (s2 | (s1 & s3) | (s12 & s6) | (s13 & s9));
endmodule

```

Verilog: Simulation Sources

The simulation of the circuit is written as the following. The test cases for the input A and B are:

- | | | | |
|-----------------------|-----------------------|-----------------------|-----------------------|
| • Test Case #1 | • Test Case #2 | • Test Case #3 | • Test Case #4 |
| A → 0000 (0) | A → 1000 (-1) | A → 0111 (+7) | A → 1001 (-7) |
| B → 1000 (-8) | B → 1111 (-8) | B → 0011 (+3) | B → 0001 (+1) |
| • Test Case #5 | • Test Case #6 | • Test Case #7 | • Test Case #8 |
| A → 0100 (+4) | A → 1110 (-2) | A → 0100 (+5) | A → 1111 (-1) |
| B → 1100 (-4) | B → 1110 (-2) | B → 0010 (+2) | B → 1111 (-1) |

```

`timescale 1ns / 1
module Sim_Comp_Signed_4Bit(
);

    // INPUTS

```

```

reg A3;
reg A2;
reg A1;
reg A0;
reg B3;
reg B2;
reg B1;
reg B0;

// OUTPUTS
wire A_GREATER_B;
wire A_LESS_B;
wire A_EQUAL_B;

Comparator_Signed_4Bit UUT (
.A3(A3),
.A2(A2),
.A1(A1),
.A0(A0),

.B3(B3),
.B2(B2),
.B1(B1),
.B0(B0),

.A_GREATER_B(A_GREATER_B),
.A_LESS_B(A_LESS_B),
.A_EQUAL_B(A_EQUAL_B)
);

// INITIALIZE INPUTS
initial begin
    // -----
    // TEST #1
    // A = 0 // B = -8
    // -----
    A3 = 0;
    A2 = 0;
    A1 = 0;
    A0 = 0;

    B3 = 1;
    B2 = 0;
    B1 = 0;
    B0 = 0;
    #10;

    // -----
    // TEST #2
    // A = -8 // B = -1
    // -----
    A3 = 1;
    A2 = 0;
    A1 = 0;
    A0 = 0;

    B3 = 1;
    B2 = 1;
    B1 = 1;
    B0 = 1;
    #10;

    // -----
    // TEST #3
    // A = +7 // B = +3
    // -----
    A3 = 0;

```

```

A2 = 1;
A1 = 1;
A0 = 1;

B3 = 0;
B2 = 0;
B1 = 1;
B0 = 1;
#10;

// -----
// TEST #4
// A = -7 // B = +1
// -----
A3 = 1;
A2 = 0;
A1 = 0;
A0 = 1;

B3 = 0;
B2 = 0;
B1 = 0;
B0 = 1;
#10;

// -----
// TEST #5
// A = +4 // B = -4
// -----
A3 = 0;
A2 = 1;
A1 = 0;
A0 = 0;

B3 = 1;
B2 = 1;
B1 = 0;
B0 = 0;
#10;

// -----
// TEST #6
// A = -2 // B = -2
// -----
A3 = 1;
A2 = 1;
A1 = 1;
A0 = 0;

B3 = 1;
B2 = 1;
B1 = 1;
B0 = 0;
#10;

// -----
// TEST #7
// A = 5 // B = 2
// -----
A3 = 0;
A2 = 1;
A1 = 0;
A0 = 0;

B3 = 0;
B2 = 0;
B1 = 1;
B0 = 0;

```

```

#10;

// -----
// TEST #8
// A = -1 // B = -1
// -----
A3 = 1;
A2 = 1;
A1 = 1;
A0 = 1;

B3 = 1;
B2 = 1;
B1 = 1;
B0 = 1;
#10;

end
endmodule

```

Verilog: Constraints

The constraints file for exporting circuit to the FPGA board are the following. Comments about the code are written in order to better explaining the code.

```

# For the constraint file, 8 switches and 3 LEDs will be needed.
# Switches for the first 4-Bit Number --> R15, M13, L16, J15
# Switches for the second 4-Bit Number --> T8, R13, U18, T18
# LED for A>B: H17
# LED for A<B: K15
# LED for A=B: J13

# -----
# INPUT SWITCHES A
# -----
# SW A3
set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { A3 }];
# SW A2
set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { A2 }];
# SW A1
set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { A1 }];
# SW A0
set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { A0 }];

# -----
# INPUT SWITCHES B
# -----
# SW B3
set_property -dict { PACKAGE_PIN T8 IOSTANDARD LVCMOS33 } [get_ports { B3 }];
# SW B2
set_property -dict { PACKAGE_PIN R13 IOSTANDARD LVCMOS33 } [get_ports { B2 }];
# SW B1
set_property -dict { PACKAGE_PIN U18 IOSTANDARD LVCMOS33 } [get_ports { B1 }];
# SW B0
set_property -dict { PACKAGE_PIN T18 IOSTANDARD LVCMOS33 } [get_ports { B0 }];

# -----
# OUTPUT LEDS
# -----
# LED A_GREATER_B

```


```

set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { A_GREATER_B }];
# LED A_LESS_B
set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { A_LESS_B }];
# LED A_EQUAL_B
set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { A_EQUAL_B }];

```

Verilog: Synthesis

 Synthesis results of the 4-Bit Signed Comparator circuit.




Utilization Post-Synthesis | Post-Implementation

[Graph](#) | [Table](#)

Resource	Estimation	Available	Utilization %
LUT	6	63400	0.01
IO	11	210	5.24

Verilog: Implementation

 Implementation results of the 4-Bit Signed Comparator circuit.



Utilization				Post-Synthesis	Post-Implementation
				Graph Table	
Resource	Utilization	Available	Utilization %		
LUT	6	63400	0.01		
IO	11	210	5.24		

Verilog: Project Summary

Project summary of the 4-Bit Signed Comparator circuit.

Project Summary
Comparator_Signed_4Bit.v
Sim_Comp_Signed_4Bit.v
Cons_Comp\$4.xdc

SettingsEdit

Project name: PreLab3_4Bit_Signed_Comparator
Project location: C:/Users/BERNA/Desktop/CS303/Vivado Xilinx Projects/PreLab3_4Bit_Signed_Comparator
Product family: Artix-7
Project part: xc7a100tcs9324-1
Top module name: Comparator_Signed_4Bit
Target language: Verilog
Simulator language: Mixed

Synthesis

Status: Complete
Messages: 1 warning
Part: xc7a100tcs9324-1
Strategy: Vivado Synthesis Defaults
Report Strategy: Vivado Synthesis Default Reports

Implementation

Status: Complete
Messages: 4 warnings
Part: xc7a100tcs9324-1
Strategy: Vivado Implementation Defaults
Report Strategy: Vivado Implementation Default Reports
Incremental compile: None

DRC Violations

Summary: 1 warning
[Implemented DRC Report](#)

Timing

Worst Negative Slack (WNS): NA
Total Negative Slack (TNS): NA
Number of Failing Endpoints: NA
Total Number of Endpoints: NA
[Implemented Timing Report](#)

Utilization

Post-Synthesis | Post-Implementation
Graph | Table

Resource	Utilization	Available	Utilization %
LUT	6	63400	0.01
IO	11	210	5.24

Power

Summary | On-Chip
Total On-Chip Power: 3.149 W
Junction Temperature: 39.4 °C
Thermal Margin: 45.6 °C (9.9 W)
Effective θJA: 4.6 °C/W
Power supplied to off-chip devices: 0 W
Confidence level: Low
[Implemented Power Report](#)