

CS303 // PRE-LAB #4 Report

Berna Yildiran 26431

Circuit Flow

The module "Mod7":

Inputs:

- `clk` : a clock input signal
- `reset` : a reset input signal
- `enable` : an enable input signal
- `configure` : a 3-bit configuration input signal
- `serial_in` : a 32-bit serial input signal

Output:

- `out` : a 3-bit mod 7 result output signal
- `cnt_out` : an output signal indicating when the count value has reached the configuration value
- `led` : an output signal that toggles when `cnt_out` is 1

Internal signals:

- `x` : a 32-bit register used to store a value that will be modified in the code
- `cnt` : a 5-bit register used to store a count value

Step by Step Circuit:

1. The module has an `always` block that is triggered on the rising edge of either the `clk` or `reset` signals. This means that the block of code inside the `always` block will execute every time either of these signals makes a transition from 0 to 1.
2. The `always` block begins by checking the value of the `reset` signal. If `reset` is 1, the code initializes the values of `x`, `cnt`, `out`, `cnt_out`, and `led` to 0.
3. If `reset` is 0, the code increments the count value stored in `cnt`, and checks if it is equal to the `configure` value. If it is, the code resets the count value to 0 and sets `cnt_out` to 1.
4. The code then checks the value of `cnt_out`. If it is 1, the code toggles the value of `led` and sets `cnt_out` back to 0.
5. Finally, the code concatenates the lower 30 bits of `x` with the `serial_in` value and stores the result in `x`. It then performs a modulo 7 operation on `x` and stores the result in `out`.

Verilog: Design Sources

The Verilog source code of the “Mod7” circuit:

```
`timescale 1ns / 1ps

////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company: Sabanci University PRE-LAB 4
// Engineer: Berna Yildiran
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module Mod7(
    input clk,
    input reset,
    input enable,

    // 3-bit configuration input
    input [2:0] configure,

    // 32-bit serial input
    input [31:0] serial_in,

    // 3-bit mod 7 result output
    output reg [2:0] out,
    output reg cnt_out,
    output reg led
);

// 32-bit register used to store a value that will modified in the code
reg [31:0] x;

// 5-bit register used to store a count value
reg [4:0] cnt;

// Always block triggered on the rising edge of the clock or reset signals
always @(posedge clk or posedge reset)
begin
    // Check the value of the reset signal
    // If reset is 1, initialize values to 0
    if (reset) begin
        x <= 0;
        cnt <= 0;
        out <= 0;
        cnt_out <= 0;
        led <= 0;
    end

    // If reset is 0, execute the following code
    else begin
        // Increment the count value
        cnt <= cnt + 1;

        // Check if the count value is equal to the configuration value
        // If so, reset the count value to 0 and set cnt_out to 1
        if (cnt == configure) begin
            cnt <= 0;
            cnt_out <= 1;
        end

        // If cnt_out is 1, toggle the value of led
        if (cnt_out) begin
            cnt_out <= 0;
            led <= ~led;
        end
    end
end
```

```

        // Concatenate the lower 30 bits of x with the serial input value and store the result in x
        // Perform a mod 7 operation on x and store the result in out
        x <= {x[30:0], serial_in};
        out <= x % 7;
    end
end
endmodule

```

Verilog: Simulation Sources

The simulation code of the circuit is written as the following:

```

`timescale 1ns / 1ps

/////////////////////////////////////////////////////////////////
// Company: Sabanci University
// Engineer: Berna Yildiran
/////////////////////////////////////////////////////////////////

module sim_Mod7;
    reg clk;
    reg reset;
    reg enable;
    reg [2:0] configure;
    reg [31:0] serial_in;
    wire [2:0] out;
    wire cnt_out;
    wire led;

    // Instantiate the div7 module
    Mod7 UUT (
        .clk(clk),
        .reset(reset),
        .enable(enable),
        .configure(configure),
        .serial_in(serial_in),
        .out(out),
        .cnt_out(cnt_out),
        .led(led)
    );

    // Initialize inputs
    initial begin
        clk = 0;
        reset = 0;
        enable = 1;
        configure = 0;
        serial_in = 0;
    end

    // Generate clock signal
    always #5 clk = ~clk;

    // Test case 1: Reset
    initial begin
        #100;
        reset = 1;
        #100;
        reset = 0;
    end
end

```

```

initial begin
    // Test case 2: Mod 7 of a 4-bit number
    #200;
    serial_in = 4'b0010; //2 --> 1
    #100;
    serial_in = 4'b0101; //5 --> 2
    #100;
    serial_in = 4'b1010; //10 --> 3
    #100;
    serial_in = 4'b1110; //14 --> 0

    //Test case 3: Mod 7 of a 5-bit number
    #100;
    serial_in = 5'b01011; //11 --> 4
    #100;
    serial_in = 5'b10011; //19 --> 5
    #100;
    serial_in = 5'b00011; //20 --> 6
    #100;
    serial_in = 5'b11000; //24 --> 0
    #100;
    serial_in = 5'b11110; //30 --> 2

    //Test case 4: Mod 7 of a 6-bit number
    #100;
    serial_in = 6'b011111; //31 --> 3
    #100;
    serial_in = 6'b100010; //34 --> 6
    #100;
    serial_in = 6'b101010; //42 --> 0
    #100;
    serial_in = 6'b101110; //46 --> 4
    #100;
    serial_in = 6'b111010; //58 --> 2
    #100;
    serial_in = 6'b111111; //63 --> 0

end
endmodule

```

Verilog: Constraints

The constraints file for exporting circuit to the FPGA board are the following:

```

# I changed "CLK100MHZ" to "clk"
# -----
# set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }];
# create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];
# -----

set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { clk }];
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {clk}];

set_property -dict { PACKAGE_PIN H6      IOSTANDARD LVCMOS33 } [get_ports { serial_in }];
set_property -dict { PACKAGE_PIN P18     IOSTANDARD LVCMOS33 } [get_ports { reset }];

set_property -dict { PACKAGE_PIN M13     IOSTANDARD LVCMOS33 } [get_ports { configure[2] }];
set_property -dict { PACKAGE_PIN L16     IOSTANDARD LVCMOS33 } [get_ports { configure[1] }];
set_property -dict { PACKAGE_PIN J15     IOSTANDARD LVCMOS33 } [get_ports { configure[0] }];

```

```

set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { out[0] }];
set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { out[1] }];
set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { out[2] }];
set_property -dict { PACKAGE_PIN V11 IOSTANDARD LVCMOS33 } [get_ports { led }];

set_property -dict { PACKAGE_PIN V10 IOSTANDARD LVCMOS33 } [get_ports { enable }];

```

Verilog Simulation Results

Waveform of the “Mod 7” circuit based on the simulation code:

 


Figure 1: Complete Waveform

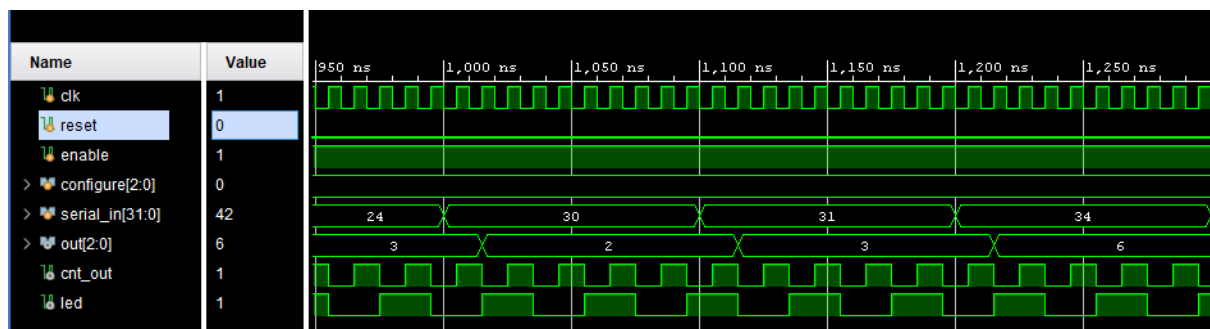


Figure 2: Zoomed in Waveform

Verilog: Synthesis

Synthesis results of “Mod 7” circuit.

 


Figure 3: Synthesis Graph

Utilization

Post-Synthesis | Post-Implementation

Graph | Table

Resource	Estimation	Available	Utilization %
LUT	120	63400	0.19
FF	42	126800	0.03
IO	42	210	20.00
BUFG	1	32	3.13

Figure 4: Synthesis Table

Verilog: Implementation

Implementation results of “Mod 7” circuit.

 


Figure 5: Implementation Graph

Utilization

Post-Synthesis | Post-Implementation

Graph | Table

Resource	Utilization	Available	Utilization %
LUT	120	63400	0.19
FF	42	126800	0.03
IO	42	210	20.00
BUFG	1	32	3.13

Figure 6: Implementation Table

Verilog: Project Summary

Project summary of the “Mod 7” circuit.

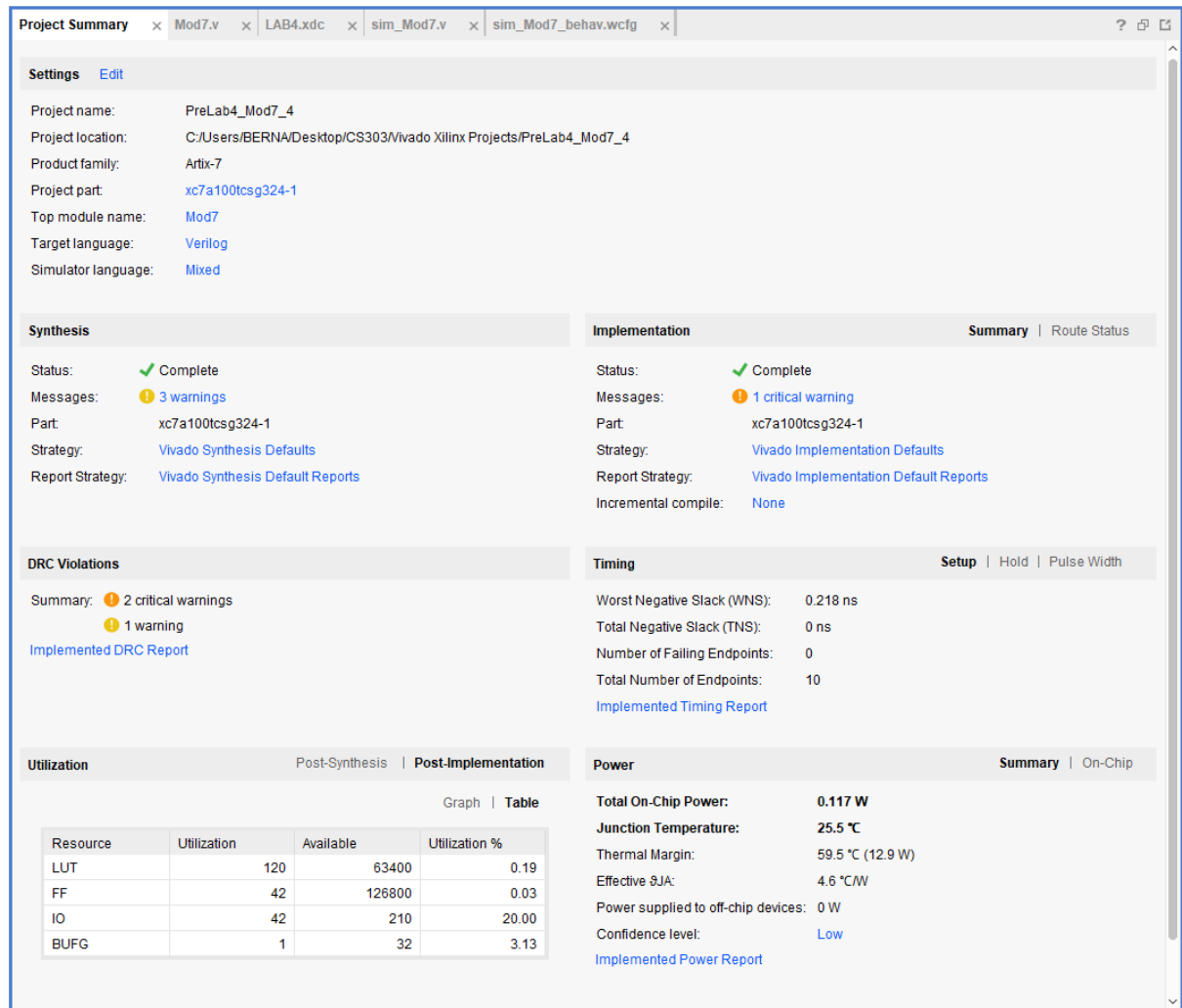


Figure 7: Project Summary